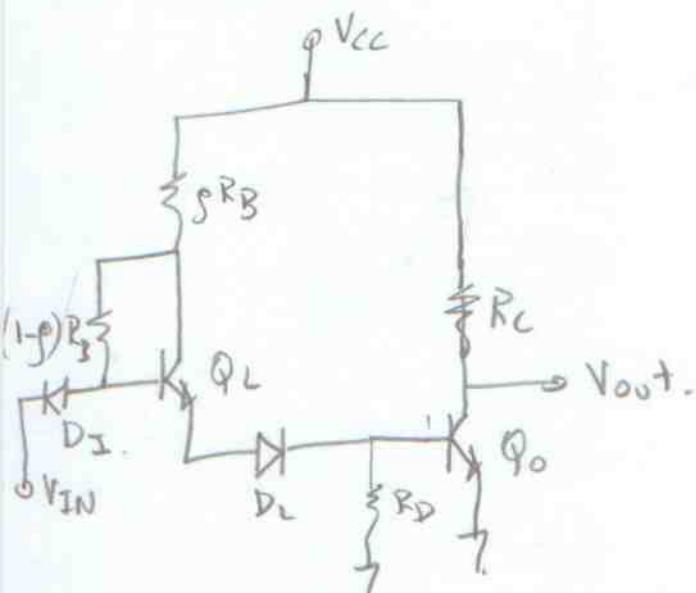


Modified DTL :



DTL with the following parameters is manufactured as 930 Series.

$$V_{CC} = 5V$$

$$gR_B = 1.75 \text{ k}\Omega; R_C = 6 \text{ k}\Omega.$$

$$(1-g) R_B = 2 \text{ k}\Omega;$$

$$R_D = 5 \text{ k}\Omega;$$

$$(g = 7/15)$$

$$0 < g < 1.$$


(Q_L : Level shifting transistor).

① Q_0 turns ON when $V_{RD} = 0.7V$; $\rightarrow V_{IN} = 1.4V$;

② Q_0 saturates (at the edge) $V_{RD} = 0.8V$; $\rightarrow V_{IN} = 1.5V$;

\leftarrow edge of conduction

\leftarrow edge of saturation.

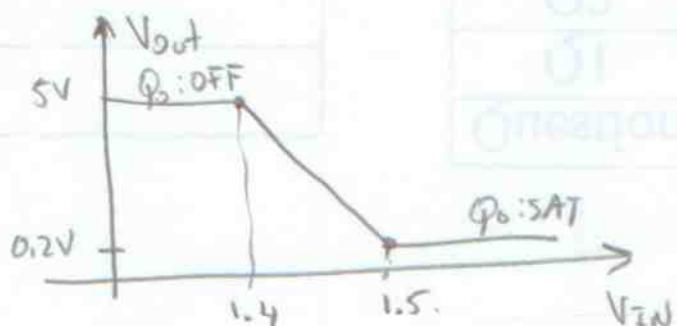

Q_L : provides more current to Q_0 since it's adjusted/biased)


in self-biased configuration and remains in FA when V_{IN} is in $[0V, 5V]$.

(Current provided by Q_0 improves Fan-out at O.L.)


"to be seen shortly"

Let's analyze self-biased configuration.

61B

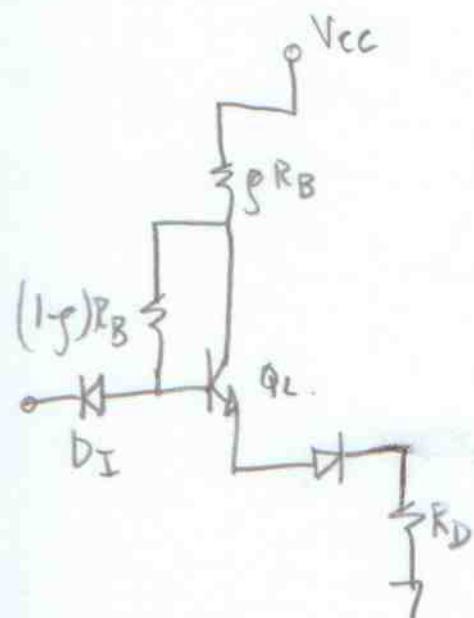


① Assume DI: OFF

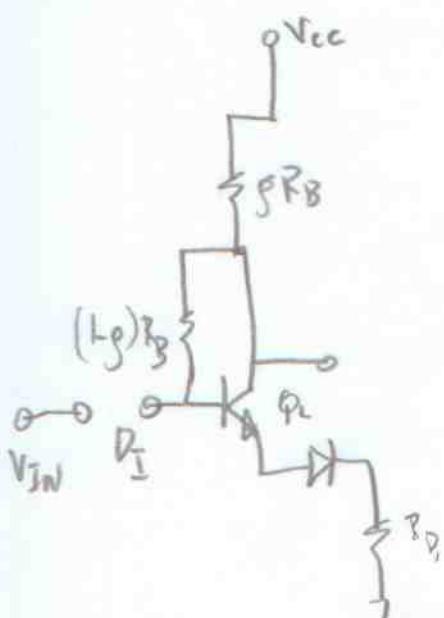


Q_L has to be in FA

(Since Assume SAT)

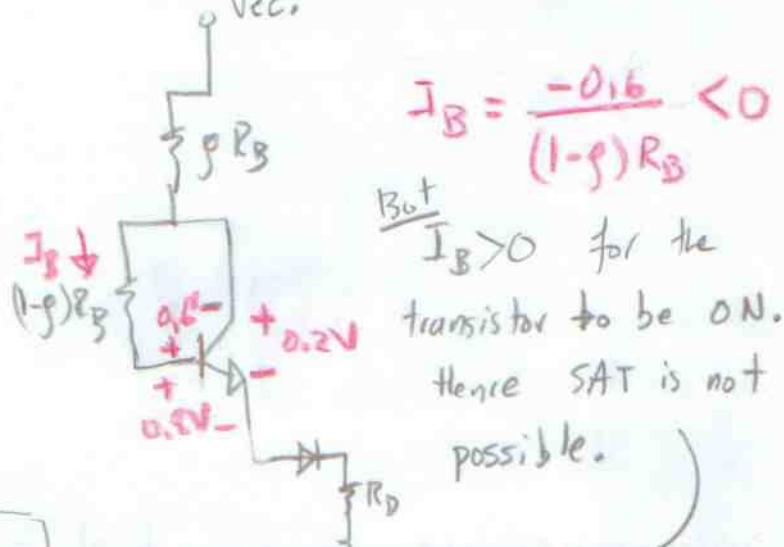

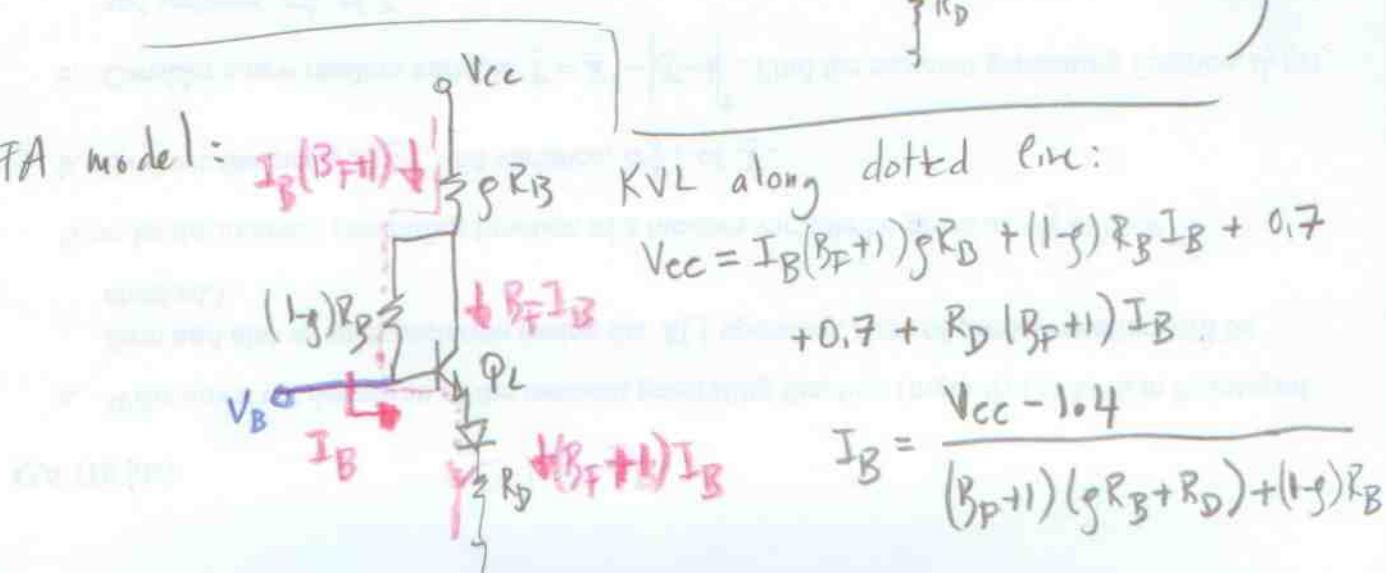
With FA model: $I_B(B_F+1) + R_F I_B$ KVL along dotted line:



Using 93D Series Parameters ($B_F = 100$)

61
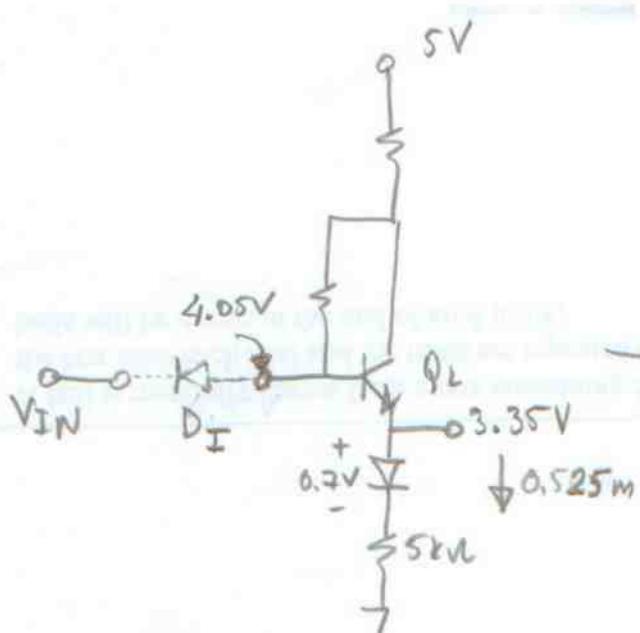
$$I_B = \frac{5 - 1.4}{(101)(6.75) + 2} \text{ mA} = 5.25 \mu\text{A}$$




Then when


$$V_{IN} > 4.05 - 0.7 = 3.35 \text{ V}$$

D_1 turns OFF and the contact of V_{IN} to Q_L is cut-off.

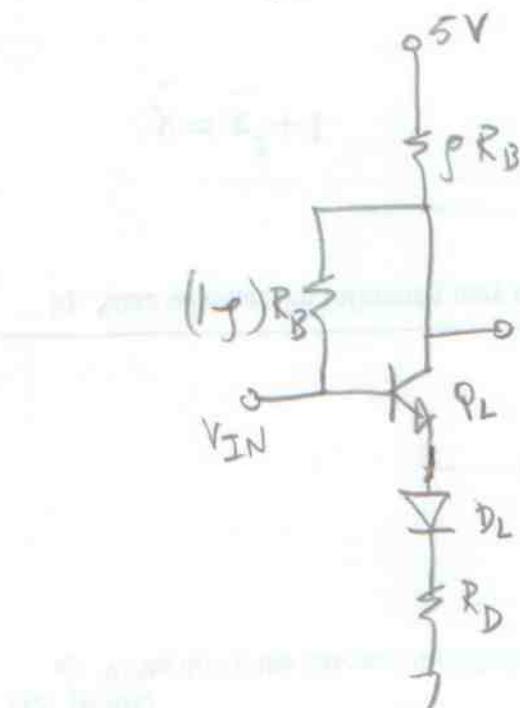As an exercise, assume that D_1 diode is removed and we have the following configuration.



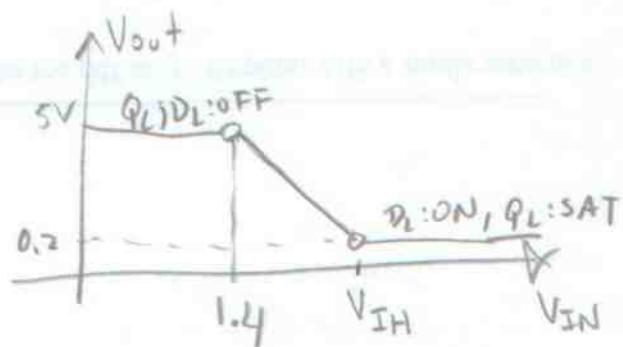
It's clear that the system has the following VTC.



Let's find V_{IH} :

63 D

Assume SAT

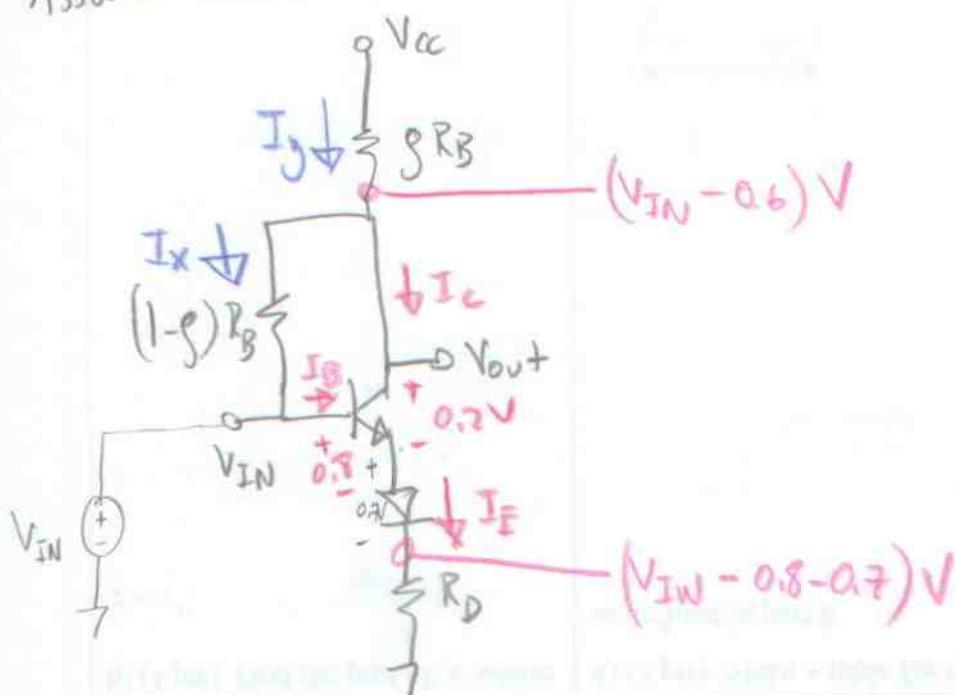

$$I_X = \frac{(V_{IN} - 0.6) - V_{IN}}{(1-g)R_B} = -\frac{0.6}{(1-g)R_B} A \quad ; \quad I_y = \frac{V_{CC} - (V_{IN} - 0.6)}{gR_B}$$

$$= \frac{V_{CC} + 0.6 - V_{IN}}{gR_B} A$$

$$I_E = \frac{V_{IN} - 1.5}{R_D} A.$$

$$I_C = I_y - I_X = \frac{V_{CC} + 0.6 - V_{IN}}{gR_B} + \frac{0.6}{(1-g)R_B} = \frac{V_{CC} - V_{IN}}{gR_B} + \frac{0.6}{g(1-g)R_B}$$

$$I_B = I_E - I_C = \frac{V_{IN} - 1.5}{R_D} - \left(\frac{V_{CC} - V_{IN}}{gR_B} + \frac{0.6}{g(1-g)R_B} \right)$$

For SAT conditions are.

$$\textcircled{1} \quad I_B > 0 \quad (\text{ON})$$

$$\textcircled{2} \quad R_P I_B > I_C. \quad (\text{Not FA})$$

Using 13D series parameters:

64/E

$$\left\{ \begin{array}{l} I_B = \frac{V_{IN} - 1.5}{5} + \frac{V_{IN} - 5}{1.75} - \frac{0.6}{15.2} \text{ mA.} \\ I_B = \frac{V_{IN}(7+20) - 100 - 10.5 - 22.5}{35} \text{ mA.} \\ I_B = \frac{27V_{IN}}{35} - \frac{132.5}{35} \text{ mA} \end{array} \right.$$


$$\left\{ \begin{array}{l} I_C = \frac{5 - V_{IN}}{7/4} + \frac{0.6}{15.2} \text{ mA} = \frac{-4V_{IN} + 20 + 4.5}{7} \\ I_C = \frac{24.5}{7} - \frac{4}{7}V_{IN} \end{array} \right.$$

SAT condition:

$$B_F I_B > I_C \rightarrow \left(\frac{27V_{IN}}{35} - \frac{132.5}{35} \right) 100 > \left(\frac{24.5}{7} - \frac{4}{7}V_{IN} \right)$$

$$20 \left(27V_{IN} - 132.5 \right) > \left(24.5 - 4V_{IN} \right)$$

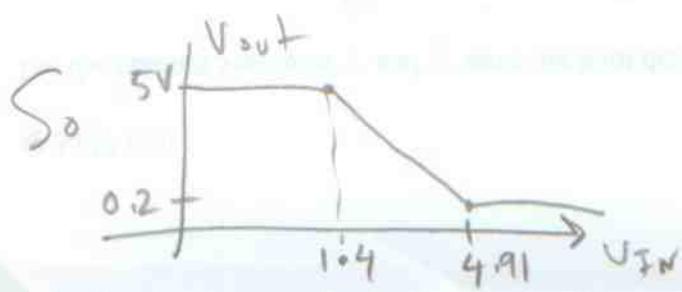
$$V_{IN} > \frac{20 \cdot (132.5) + 24.5}{544}$$



$$V_{IN} > 4.91V$$

This concludes the exercise.

Thn

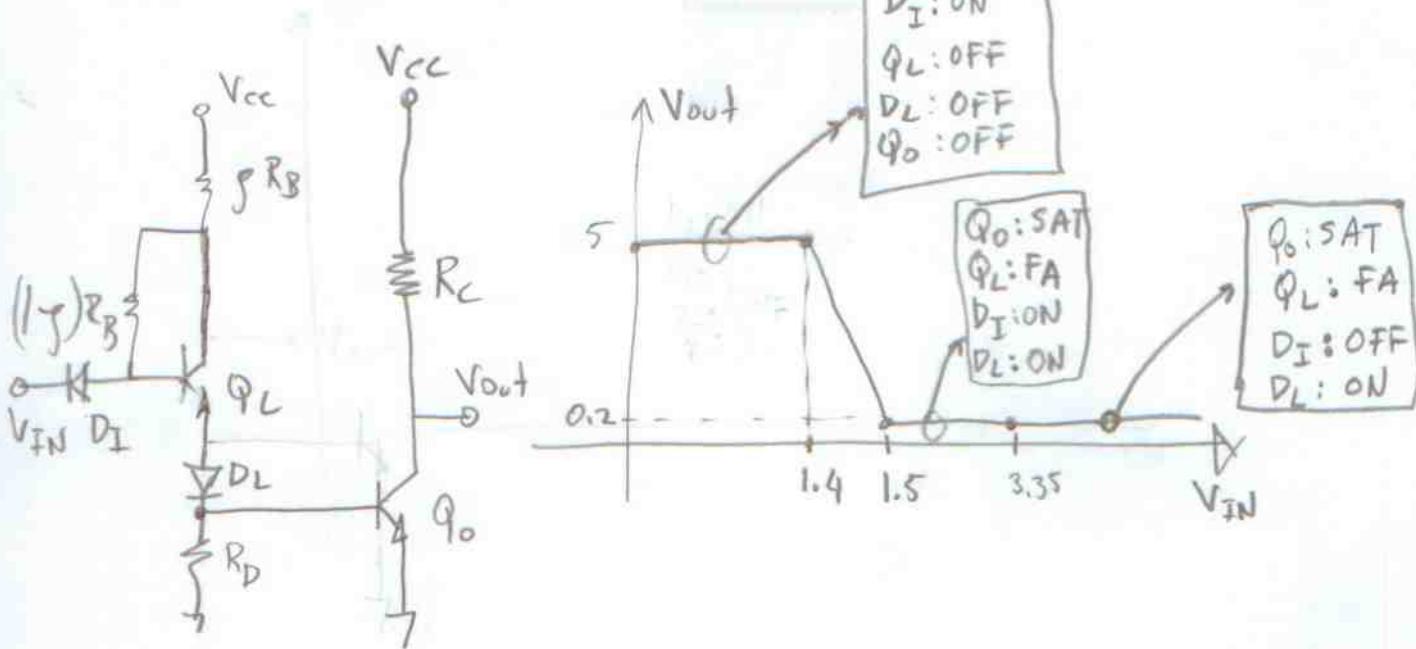

Note that

